

Block diagram


{Top View}

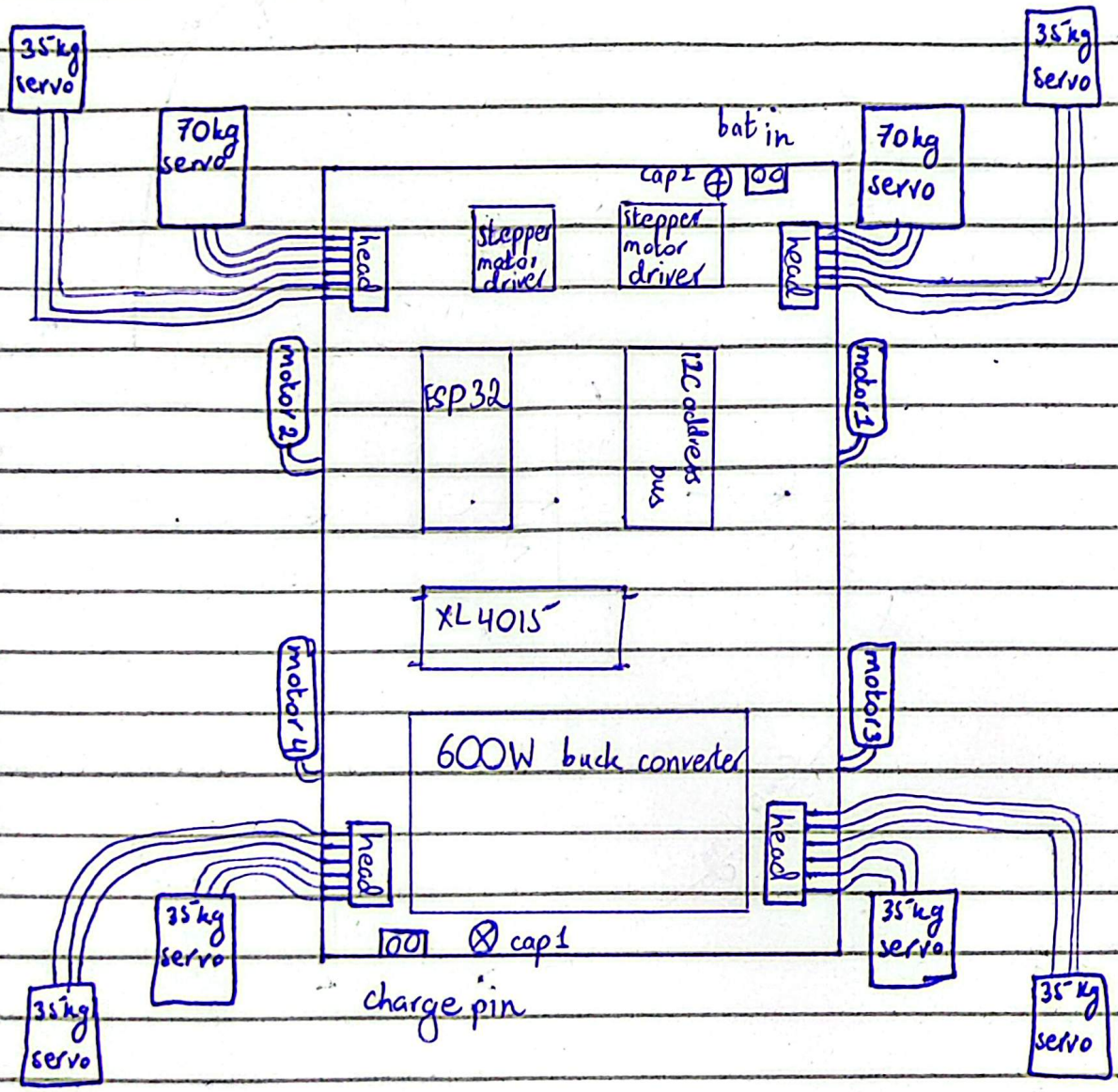

Project Wiring Sub-diagram

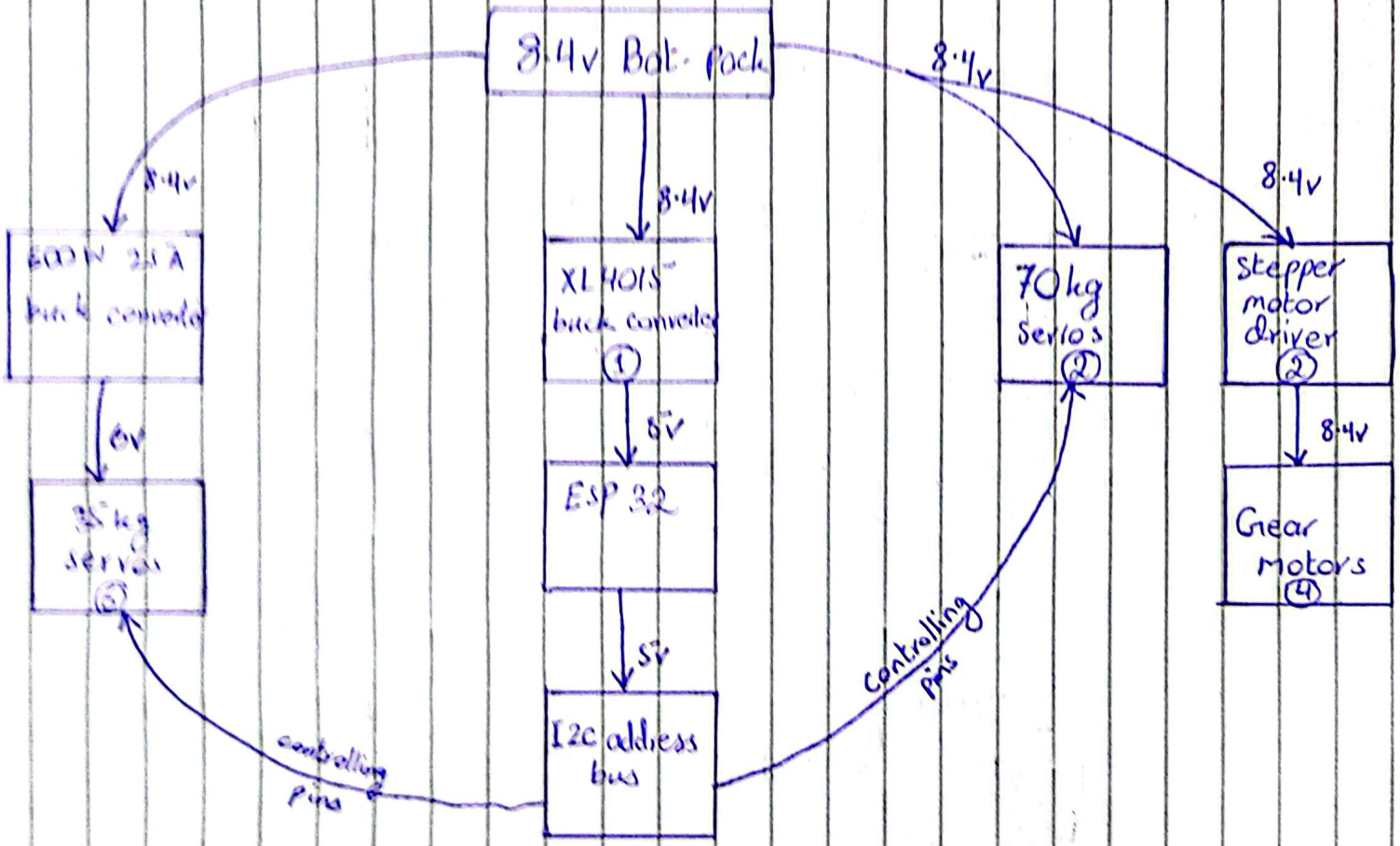

Robo dog -V-1

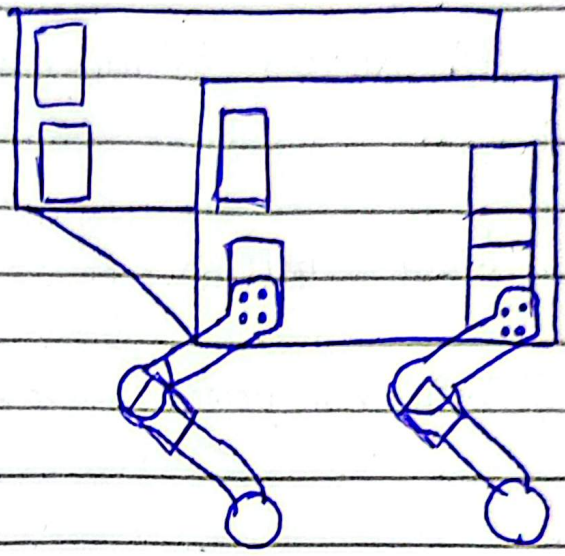

Total servos

8 servos

(2) servos are 70kg 180° rotation

intake = 8.4V

(6) Servos are 35kg 180° rotation

intake = 6V

Total motors

(4) yellow gear motors

intake = 8.4V

MicroController

esp 32

intake = 5V

Power modules	Use Case
XL4015 5V buck converter	Power Esp32 stable 5V input.
Lithium battries	Giving Output for 8.4v to Serro
DC-DC high power Converter	Power providing of stable current max at 25Amps for 6 serros giving 6v.

Drivers and [redacted] Addressers

Stepper motor driver

two used as one can control two motors

Provide direct 8.4v

16 channel servo Address

for all 8 servos

Power throug Esp32